

CO20-320241

**Computer Architecture and
Programming Languages**

CAPL

Lecture 18 & 19


Dr. Kinga Lipskoch

Fall 2019

Executing Branch Operations

Branch operations involve:

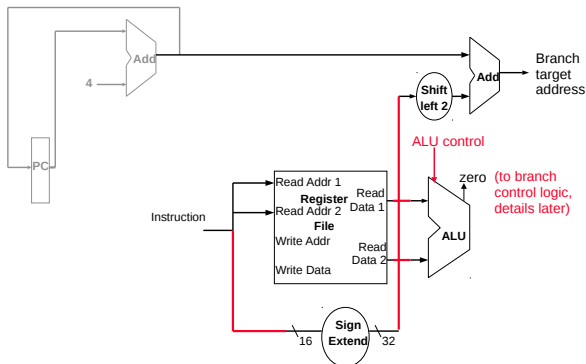
- ▶ compare the operands read from the Register File during decode for equality (**zero** ALU output)
- ▶ compute the branch target address by adding the updated PC to the 16-bit signed-extended offset field in the instruction



Executing Jump Instructions

Jump operations involve:

 
- ▶ replace the lower 28 bits of the PC with the lower 26 bits of the fetched instruction shifted left by 2 bits



Creating a Single Datapath from the Parts

- ▶ Assemble the datapath segments and add control lines and multiplexors as needed
- ▶ **Single cycle** design – fetch, decode and execute each instruction in **one** clock cycle
 - ▶ no datapath resource can be used more than once per instruction, so some must be duplicated (e.g., separate Instruction Memory and Data Memory, several adders)
 - ▶ **multiplexers** needed at the input of shared elements with control lines to do the selection
 - ▶ write signals to control writing to the Register File and Data Memory
- ▶ Cycle time is determined by length of the longest path

Fetch, R, and Memory Access Portions

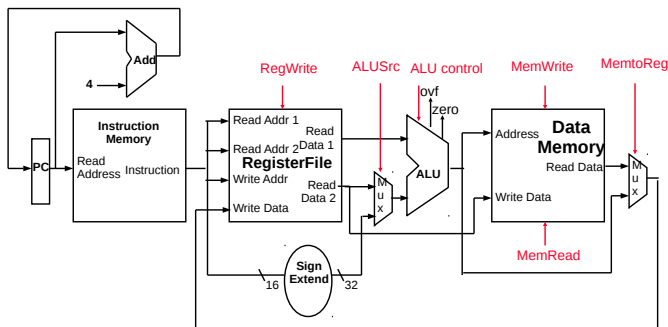

- ▶ arithmetic-logical instr. use ALU with input from two registers
- ▶ memory instr., second input is sign-extended 16-bit offset field
- ▶ value in destination register comes either from ALU (R-type) or memory (load)

ALU Control

Four bits used for control inputs:

- ▶ Only 6 of 16 bit combinations are used

ALU control lines	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set on less than
1100	NOR

- ▶ R-type: AND, OR, subtract or set on less than
- ▶ Memory: add
- ▶ Branch equal: subtraction

ALU Control Bits

Instruction opcode	ALUOp	Instruction operation	Funct field	Desired ALU action	ALU control input
LW	00	load word	XXXXXX	add	0010
SW	00	save word	XXXXXX	add	0010
Branch equal	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
R-type	10	subtract	100010	subtract	0110
R-type	10	AND	100100	and	0000
R-type	10	OR	100101	or	0001
R-type	10	set on less than	101010	set on less than	0111

- ▶ Opcode determines setting of ALUOp bits
- ▶ When ALUOp is 00 or 01, ALU action does not depend on function field
- ▶ When ALUOp is 10, function code is used to set ALU control input


Truth Table for the Four ALU Control Bits

ALUOp		Funct field						Operation
ALUOp1	ALUOp2	F5	F4	F3	F2	F1	F0	
0	0	X	X	X	X	X	X	0010
X	1	X	X	X	X	X	X	0110
1	X	X	X	0	0	0	0	0010
1	X	X	X	0	0	1	0	0110
1	X	X	X	0	1	0	0	0000
1	X	X	X	0	1	0	1	0001
1	X	X	X	1	0	1	0	0111

- ▶ X are “don't care items”
- ▶ Such a truth table can be easily turned into gates (therefore encoded in hardware)

Adding the Control

- ▶ Selecting the operations to perform (ALU, Register File and Memory read/write)
- ▶ Controlling the flow of data (multiplexor inputs)
- ▶ **Observations:**
- ▶ op field always in bits 31 – 26
- ▶ addr. of registers to be read are always specified by the rs field (bits 25 – 21) and rt field (bits 20 – 16); for lw and sw, rs is the base register
 - ▶ addr. of register to be written is in one of two places – in rt (bits 20 – 16) for lw; in rd (bits 15 – 11) for R-type instructions
 - ▶ offset for beq, lw, and sw always in bits 15 – 0

 


Summary of Control Lines

- ▶ **RegDest**
Source of the destination register for the operation
- ▶ **RegWrite**
Enables writing a register in the register file
- ▶ **ALUsrc**
Source of second ALU operand, can be a register or part of the instruction
- ▶ **PCsrc**
Source of the PC (increment $[PC + 4]$ or branch)
- ▶ **MemRead/MemWrite**
Reading/Writing from memory
- ▶ **MemtoReg**
Source of write register contents

The Seven Control Signals

Signal name	Effect when deasserted	Effect when asserted
RegDst	The register destination number for the Write register comes from the rt field (bits 20:16)	The register destination number for the Write register comes from the rd field (bits 15:11).
RegWrite	None.	The register on the Write register input is written with the value on the Write data input.
ALUSrc	The second ALU operand comes from the second register file output (Read data 2)	The second ALU operand is the sign-extended, lower 16 bits of the instruction.
PCSrc	The PC is replaced by the output of the adder that computes the value of $PC + 4$.	The PC is replaced by the output of the adder that computes the branch target.
MemRead	None.	Data memory contents designated by the address input are put on the Read data output.
MemWrite	None.	Data memory contents designated by the address input are replaced by the value on the Write data input.
MemtoReg	The value fed to the register Write data input comes from the ALU.	The value fed to the register Write data input comes from the data memory.

Single Cycle Datapath with Control Unit

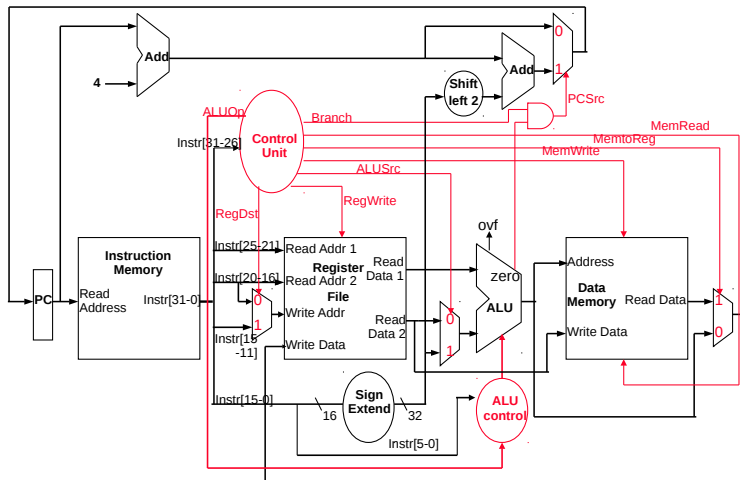


Control Lines


Instruction	RegDst	ALUSrc	Memto-Reg	Reg Write	Mem Read	Mem Write	Branch	ALUOp1	ALUOp2
R-Format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

The setting of the control lines is completely determined by the opcode fields of the instruction


R-type Instruction Data/Control Flow

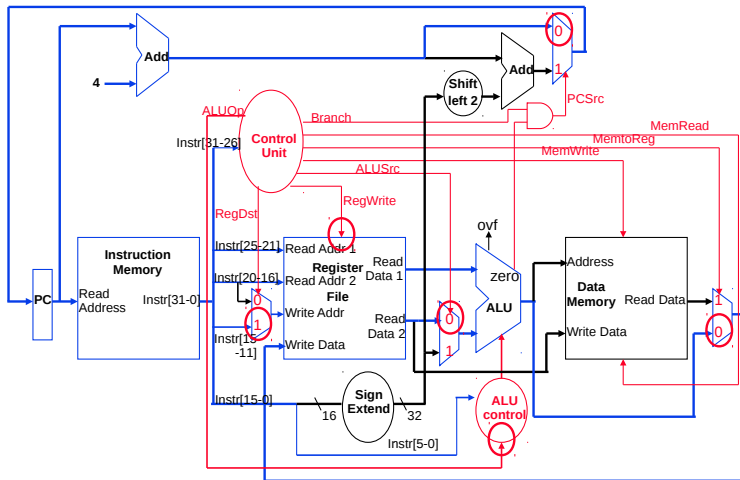


Load Word Instruction Data/Control Flow

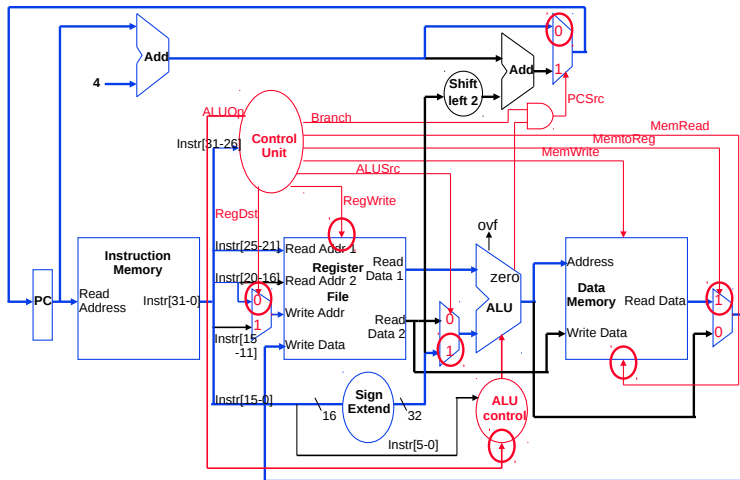

Branch Instruction Data/Control Flow

 

Adding the Jump Operation

 

Latencies in the Datapath (1)

Latency = a measure of the time delay experienced by a system

First a few notations:

- ▶ I-Mem = Instruction Memory
- ▶ D-Mem = Data Memory
- ▶ ALU = Arithmetic Logic Unit
- ▶ Add = Adder
- ▶ Mux1, Mux2, Mux3, Mux4 = 4 different multiplexors (which are in the datapath figure)
- ▶ Sign-Extent
- ▶ Shift-left-2
- ▶ RegF = Register File
- ▶ WBack = Write Back to the Register File

Latencies in the Datapath (2)

All possible paths for different instruction classes:

- ▶ ALU operations like add, etc.
- ▶ Possible paths for ALU operations:
 1. I-Mem \rightarrow RegF \rightarrow ALU \rightarrow Mux3 \rightarrow WBack to RegF
 2. I-Mem \rightarrow RegF \rightarrow Mux2 \rightarrow ALU \rightarrow Mux3 \rightarrow WBack to RegF
 3. I-Mem \rightarrow Mux1 \rightarrow RegF (Write address)
 4. Add \rightarrow Mux4 \rightarrow PCWrite (update PC)
- ▶ Depending the latencies given, you need to select the longest path in terms of time

Latencies in the Datapath (3)

- ▶ The `sw` instruction:
- ▶ Possible paths for `sw`:
 1. I-Mem \rightarrow RegF \rightarrow ALU \rightarrow D-Mem
 2. I-Mem \rightarrow RegF \rightarrow D-Mem
 3. I-Mem \rightarrow Sign-Extend \rightarrow Mux2 \rightarrow ALU \rightarrow D-Mem
 4. Add \rightarrow Mux4 \rightarrow PCWrite (update PC)
- ▶ Depending the latencies given, you need to select the longest path in terms of time

Latencies in the Datapath (4)


- ▶ The `lw` instruction:
- ▶ Possible paths for `lw`:
 1. I-Mem \rightarrow RegF \rightarrow ALU \rightarrow D-Mem \rightarrow Mux3 \rightarrow WBack to RegF
 2. I-Mem \rightarrow Mux1 \rightarrow RegF (Write address)
 3. I-Mem \rightarrow Sign-Extend \rightarrow Mux2 \rightarrow ALU \rightarrow D-Mem \rightarrow Mux3 \rightarrow WBack to RegF
 4. Add \rightarrow Mux4 \rightarrow PCWrite (update PC)
- ▶ Depending the latencies given, you need to select the longest path in terms of time

Latencies in the Datapath (5)

- ▶ Branching instructions, for example beq:
- ▶ Possible paths for beq:
 1. I-Mem \rightarrow RegF \rightarrow ALU \rightarrow Mux4 \rightarrow PCWrite (update PC)
 2. I-Mem \rightarrow RegF \rightarrow Mux2 \rightarrow ALU \rightarrow Mux4 \rightarrow PCWrite (update PC)
 3. I-Mem \rightarrow Sign-Extend \rightarrow Shift-left-2 \rightarrow Add \rightarrow Mux4 \rightarrow PCWrite (update PC)
 4. Add \rightarrow Mux4 \rightarrow PCWrite (update PC)
- ▶ Depending the latencies given, you need to select the longest path in terms of time

Single Cycle Disadvantages & Advantages

 - ▶ Uses the clock cycle inefficiently – the clock cycle must be timed to accommodate the slowest instruction
- ▶ Especially problematic for more complex instructions like floating point multiply



- ▶ May be wasteful of area since some functional units (e.g., adders) must be duplicated since they can not be shared during a clock cycle


But, it is simple and easy to understand

Multicycle Datapath Approach (1)

- ▶ Let an instruction take more than 1 clock cycle to complete
 - ▶ Break up instructions into steps where each **step** takes a cycle while trying to
 - ▶ balance the amount of work to be done in each step
 - ▶ restrict each cycle to use only one major functional unit
 - ▶ Not every instruction takes the **same** number of clock cycles
- ▶ In addition to **faster** clock rates, multicycle allows functional units that can be used more than once per instruction as long as they are used on different clock cycles, as a result
 - ▶ only need one memory – but only one memory access per cycle
 - ▶ need only one ALU/adder – but only one ALU operation per cycle

Multicycle Datapath Approach (2)

 - ▶ At the end of a cycle
 - ▶ Store values needed in a later cycle by the current instruction in an internal register (not visible to the programmer). All (except IR) hold data only between a pair of adjacent clock cycles (no write control signal needed)



IR - Instruction Register

A, B - regfile read data registers

MDR - Memory Data Register

ALUout - ALU output register

- ▶ Data used by subsequent instructions are stored in programmer visible registers (i.e., register file, PC, or memory)

Additional Registers Needed

- ▶ Data used by the same instruction must be stored in additional registers
 - ▶ Position is determined by two factors
 - ▶ which units fit into same clock cycle
 - ▶ what data is needed for later cycles
 - ▶ Instruction register (IR) and Memory data register (MDR) added to save output of the memory for instruction read and data read
 - ▶ A and B registers added to hold register operand values read from register file
 - ▶ ALUOut register holds the output of ALU
- ▶ All registers (except IR) will hold data just between a pair of adjacent cycles, thus do not need write control signal

Multicycle Datapath


- ▶ Functional units shared for different purposes
 - ▶ Multiplexer needed for Memory access
 - ▶ PC or ALUOut
 - ▶ Three ALUs replaced by one
 - ▶ additional multiplexer for first ALU input (A or PC) added
 - ▶ 4-way multiplexer for second ALU input
- ▶ More registers and multiplexers, but
- ▶ Less memory units (1 instead of 2)
- ▶ Fewer adders (2)
- ▶ Reduced hardware cost

More Control Lines Needed

- ▶ Multiple clock cycles per instruction
 - ▶ State units (PC, memory, registers) need write control lines
 - ▶ Memory needs read signal
 - ▶ Additional multiplexers need control line, 4-way needs 2
- ▶ PC has three possible sources
 - ▶ PCWrite, unconditional write of PC
 - ▶ PCWriteCond, cause write of PC, if branch is true

Actions of the 1-bit control signals		
Signal name	Effect when deasserted	Effect when asserted
RegDst	The register destination number for the Write register comes from the rt field (bits 20:16)	The register destination number for the Write register comes from the rd field (bits 15:11).
RegWrite	None.	The register on the Write register input is written with the value on the Write data input.
ALUSrcA	The first ALU operand comes from the PC.	The first ALU operand comes from the A register.
MemRead	None.	Content of memory at the location specified by the Address input is put on Memory data output.
MemWrite	None.	Memory contents at the location specified by the Address input is replaced by value on Write data input.
MemtoReg	The value fed to the register Write data input comes from the ALUOut.	The value fed to the register Write data input comes from the MDR.
lOrD	The PC is used to supply the address to the memory unit.	ALUOut is used to supply the address to the memory unit.
IRWrite	None.	The output of the memory is written into the IR.
PCWrite	None.	The PC is written; the source is controlled by PCSource.
PCWriteCond	None.	The PC is written if the Zero output from the ALU is also active.
Actions of the 2-bit control signals		
Signal name	Value (binary)	Effect
ALUOp	00	The ALU performs an add operation.
	01	The ALU performs an subtract operation.
	10	The funct field of the instruction determines the ALU operation
ALUSrcB	00	The second input to the ALU comes from the B register.
	01	The second input to the ALU is the constant 4.
	10	The second input to the ALU is the sign-extended, lower bits of the IR.
	11	The second input to the ALU is the sign-extended, lower bits of the IR shifted left 2 bits.
PCSource	00	Output of the ALU (PC+4) is sent to the PC for writing.
	01	The contents of ALUOut (branch target address) are sent to the PC for writing.
	10	The jump target address (IR[25:0]) shifted left 2 bits and concatenated with PC+4[31:28] is sent to the PC for writing.

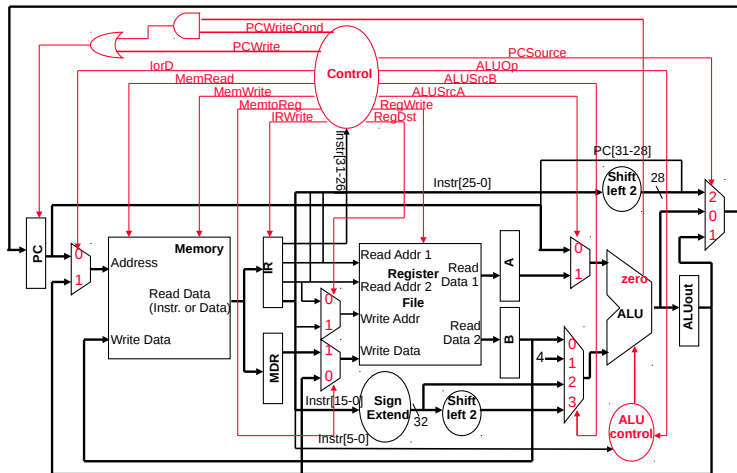The Multicycle Datapath with Control Signals



Instructions from ISA Perspective

- ▶ Move from one-cycle to multi-cycle
 - ▶ Identifying steps that take one cycle
 - ▶ Equal distribution of execution time
 - ▶ At most one operation for each of the modules
 - ▶ ALU
 - ▶ Register file
 - ▶ Memory
- ▶ New registers if
 - ▶ The signal is computed in one cycle and used in another cycle
 - ▶ The inputs of the block generating the signal may change in the second cycle


The Five Execution Steps

1. Instruction fetch
 - ▶ Move the instruction from the instruction memory to the instruction register IR
2. Instruction decode and register fetch
 - ▶ Provide the register contents for the ALU
3. Execution, memory address computation or branch completion
4. Memory access or R-type instruction completion
5. Write back step

Step 1: Instruction Fetch (1)

- ▶ Load instruction from memory
 $IR = \text{Memory}[PC]$
 - ▶ Set Read address mux (lorD) = 0 select instruction
 - ▶ Set MemRead = 1
 - ▶ Set IRWrite = 1
- ▶ Increment PC
 $PC = PC + 4$
 - ▶ Set ALUSrcA = 0 get operand from IR
 - ▶ Set ALUSrcB = 01 get operand '4'
 - ▶ Set ALUOp = 00 add
 - ▶ Allow storing new PC in PC register

Step 1: Instruction Fetch (2)

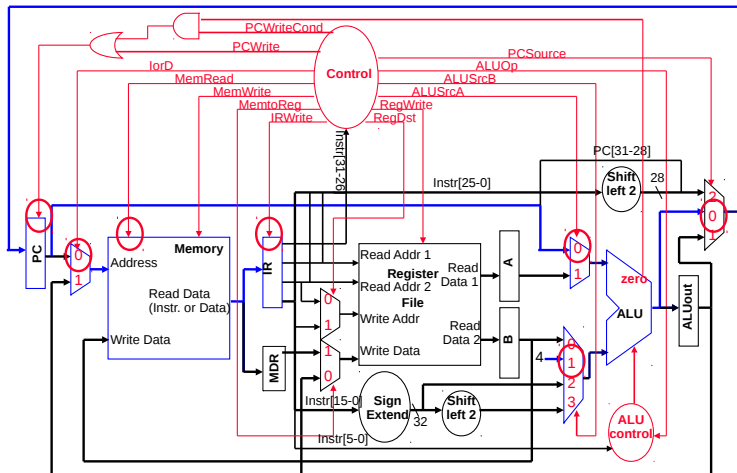

Step 2: Instruction Decode & Register Fetch (1)


- ▶ Switch registers to the output of the register block

A <= **register** [IR [25:21]] rs

B <= **register** [IR [20:16]] rt

- ▶ No signal setting required
- ▶ (Always) calculate the branch target address
ALUOut <= PC + (sign-ext. (IR [15:0]) << 2)
 - ▶ Value can just be ignored if instruction is not branch
 - ▶ Stored in the ALUOut register
 - ▶ Set ALUSrcB = 11
 - ▶ Set ALUOp = 00 add

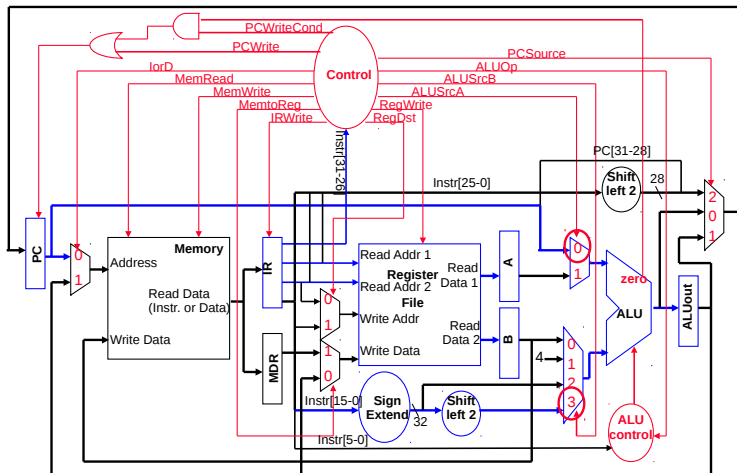
Step 2: Instruction Decode & Register Fetch (2)



Step 3: Execution, Memory Address Computation or Branch Completion

- ▶ **First** cycle where step depends on the instruction
- ▶ Selection performed by interpretation of the op + function field of the instruction
- ▶ **Memory reference**
 - ▶ calculate address
 $ALUOut \leq A + \text{sign-extend}(IR[15:0])$
 - ▶ Set $ALUSrcA = 1$ get operand from A
 - ▶ Set $ALUSrcB = 10$ get operand from sign extension unit
 - ▶ Set $ALUOp = 00$ add

Step 3: Memory Reference

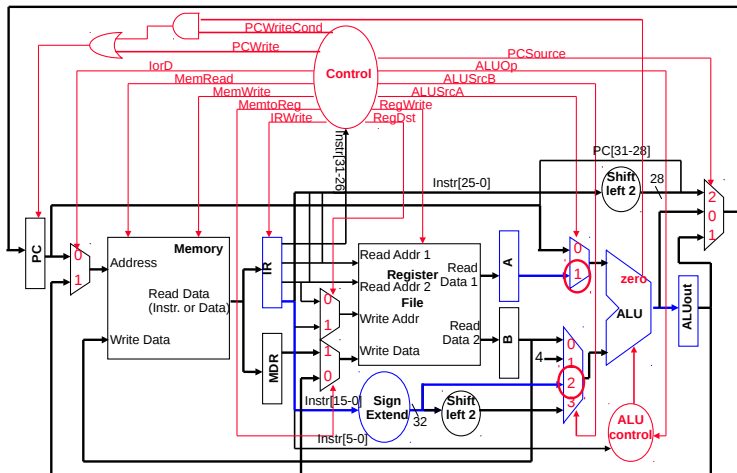


Step 3: Execution, Memory Address Computation or Branch Completion

Arithmetic-logical instruction (R-type):

$ALUOut = A \text{ op } B$

- ▶ Set $ALUSrcA = 1$ get operand from A
- ▶ Set $ALUSrcB = 00$ get operand from B
- ▶ Set $ALUOp = 10$ code from IR

Step 3: Arithmetic-Logical Instruction

 


Step 3: Execution, Memory Address Computation or Branch Completion

Branch:

`if (A == B) PC <= ALUOut`

- ▶ Set `ALUSrcA = 1` get operand from A
- ▶ Set `ALUSrcB = 00` get operand from B
- ▶ Set `ALUOp = 01` subtraction
- ▶ Write `ALUOut` to PC register

Step 3: Branch

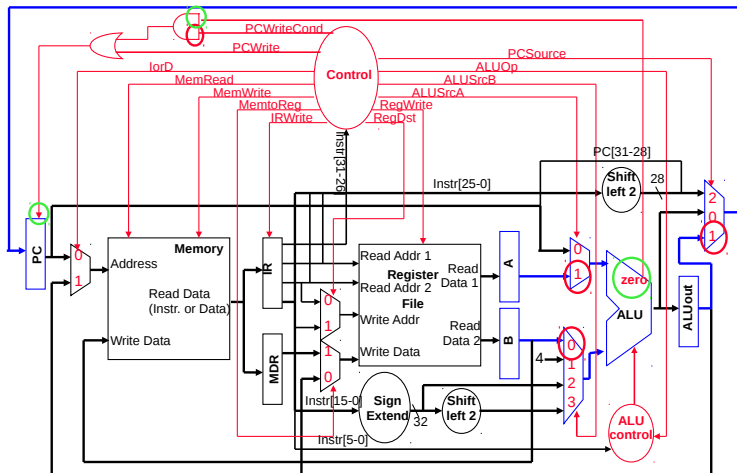


Step 3: Execution, Memory Address Computation or Branch Completion

Jump:

$PC \leq \{PC[31:28], (IR[25:0] \ll 2)\}$

Step 3: Jump

 


Step 4: Memory Access or R-type Instruction Completion


Memory reference:

- ▶ ALU controls must remain stable
- ▶ Set $lorD = 1$ address from ALU
- ▶ load from memory
MDR \leftarrow memory[ALUOut]
 - ▶ Set MemRead = 1
- ▶ store to memory
memory[ALUOut] \leftarrow B
 - ▶ Set MemWrite = 1

Step 4: Memory Reference (load word)

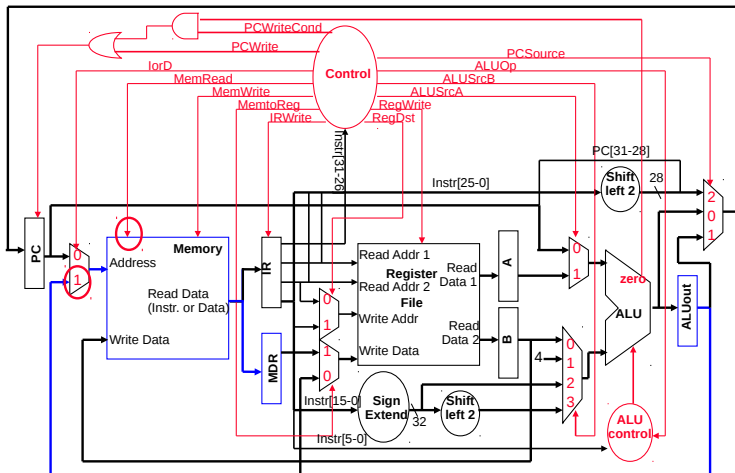

Step 4: Memory Reference (save word)

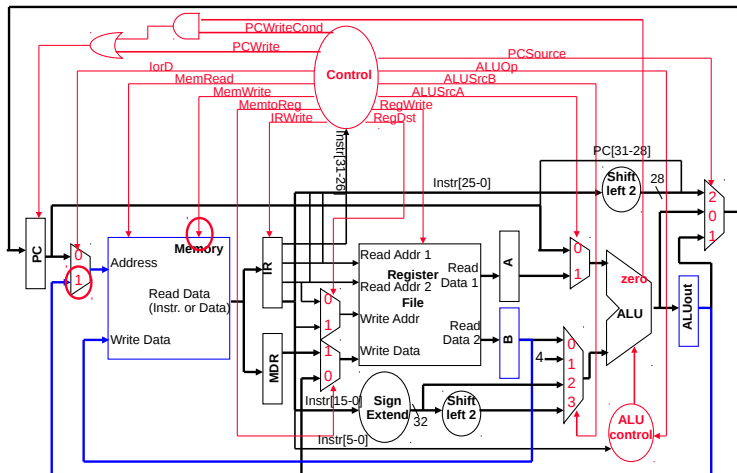


Step 4: Memory Access or R-type Instruction Completion

Arithmetic-logical instruction completion:

`Register[IR[15:11]] <= ALUOut`

- ▶ Set `RegDst = 1` Select write register
- ▶ Set `RegWrite = 1` Allow write operation
- ▶ Set `MemToReg = 0` Select ALU data
- ▶ `ALUOp, ALUSrcA, ALUSrcB = constant`

 Step 4: Arithmetic-Logical Instruction Completion



Step 5: Write Back

Write data from memory to the register:

`Register[IR[20:16]] <= MDR`

- ▶ Set `RegDst = 0` Select write `rt` as target register
- ▶ Set `RegWrite = 1` Allow write operation
- ▶ Set `MemToReg = 1` Select Memory data
- ▶ `ALUOp, ALUSrcA, ALUSrcB = constant`

Step 5: Memory Reference (load word)

